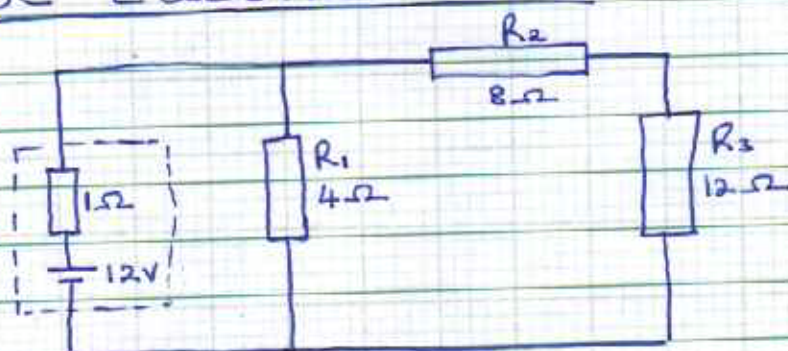


DC Electric Current


1.



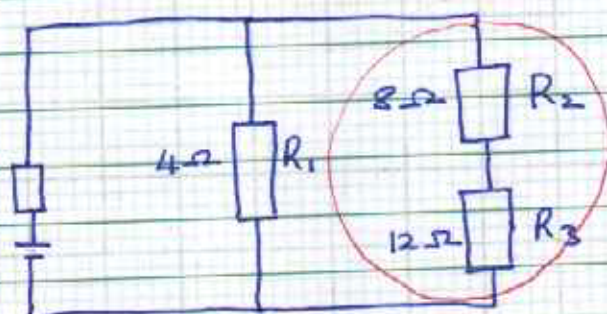
(i) Battery current, I

$$I = \frac{\text{Terminal Voltage, } V}{\text{Total Resistance } (R+r)} \quad \checkmark \textcircled{1}$$

Resistor R_2 and R_3 are in series.
Reason: They are in the same loop and connected in series.


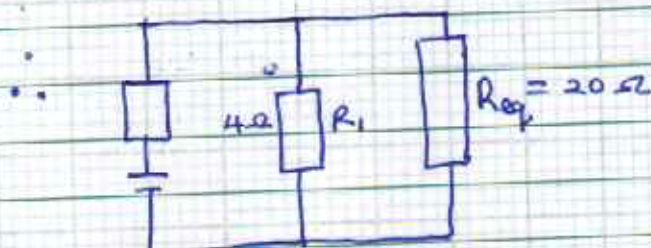
$$R_{\text{equivalent}} = R_2 + R_3 = 8\Omega + 12\Omega = 20\Omega \quad \checkmark \textcircled{1}$$




Combining R_1 and R_{eq} ; They are parallel

$$\therefore \frac{1}{R_{\text{resultant}}} = \frac{1}{R_1} + \frac{1}{R_{eq}} = \frac{1}{4\Omega} + \frac{1}{20\Omega}$$

$$\Rightarrow \frac{1}{R_r} = \frac{24}{80} \Rightarrow R_r = \frac{80}{24} = 3.3\Omega \quad \checkmark \textcircled{1}$$

Then we have:

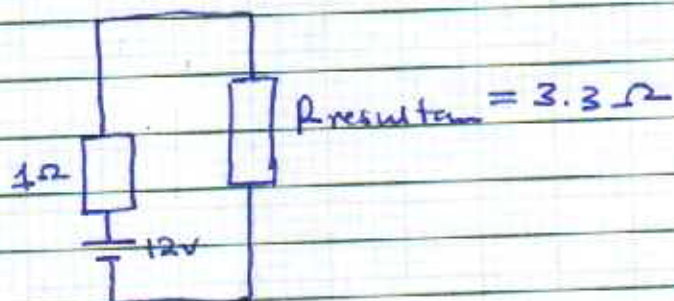

$$\therefore \text{Current, } I = \frac{\mathcal{E} = 12V}{R + r} = \frac{12V}{3.3 + 1}$$

$$I = \frac{12}{4.3} = 2.79 \text{ A}$$

(ii) Terminal voltage = $I \times R$ ✓ ①
 $= 2.79 \times 3.3$
 $= 9.23 \text{ V}$ ✓ ①


R — external resistance
 r — internal resistance.

and $\mathcal{E} = I(R + r)$

or $\mathcal{E} = V + Ir$

where $V = IR$

(iii)

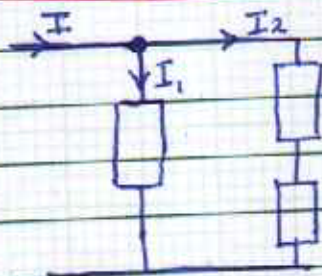

At the junction, the current, I is split into I_1 and I_2 depending on the ratio of resistors.

$$\therefore I_1 = \frac{20}{24} \times 2.79 = 2.325 \text{ A}$$

\therefore Voltage across 4Ω resistor = $I_1 \times 4\Omega$

$$\therefore V = 2.325 \times 4 \Omega$$

$$= 9.3 \text{ V}$$

I_2 is the current through both 8Ω and 12Ω resistor.

$$I_2 = \frac{4}{24} \times 2.79 = 0.465 \text{ A}$$

Voltage across the 8Ω resistor

$$V = I_2 \times 8 \Omega$$

$$= 0.465 \times 8 \Omega$$


$$= 3.72$$

Voltage across the 12Ω resistor

$$V = I_2 \times 12 \Omega$$

$$= 0.465 \times 12$$

$$= 5.58$$

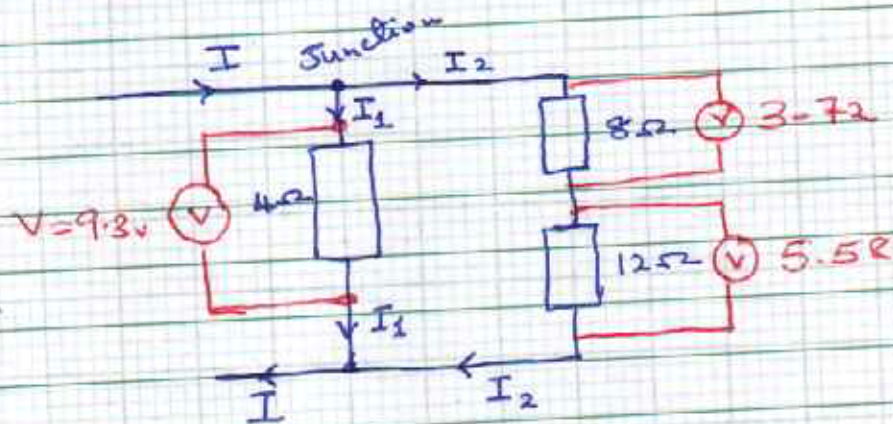

NB/ The question is testing the Kirchhoff's Law of current at the junction.